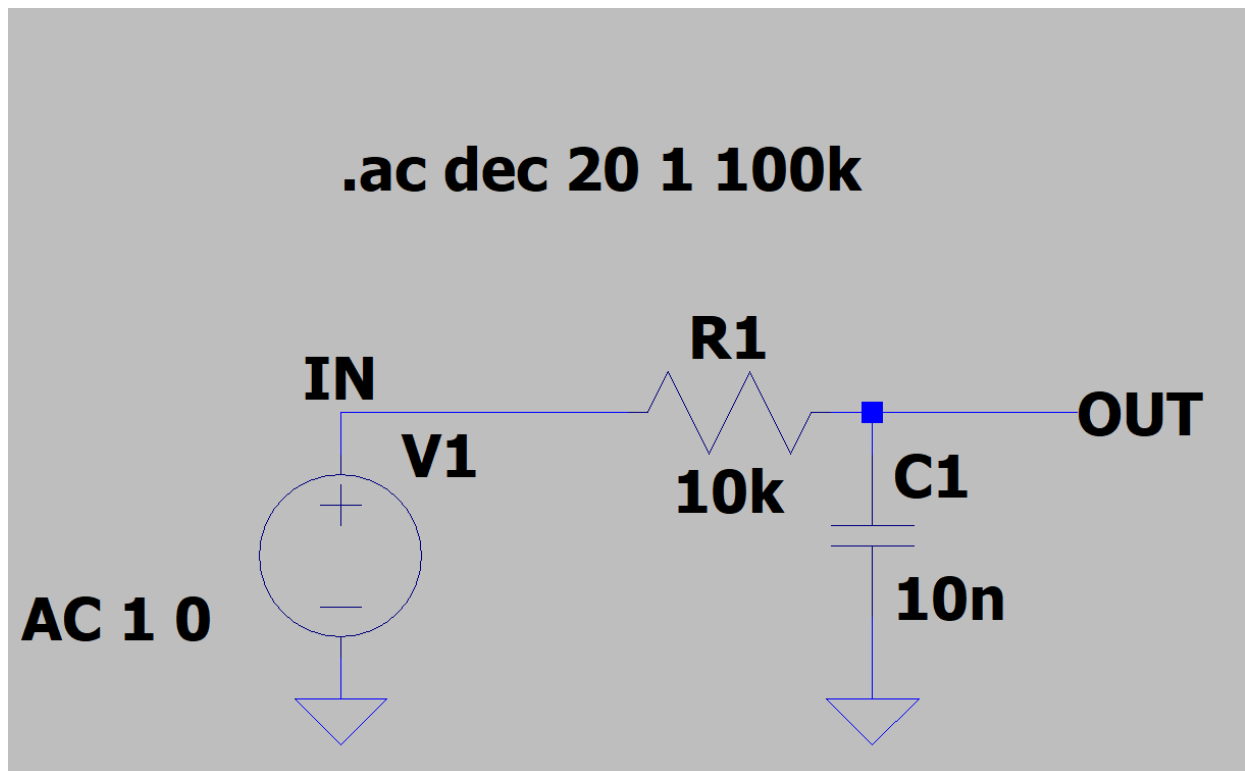


🔧 Electrical Engineering Interview Q's:


- 1 What kind of filter is this? 🧑🔧
- 2 What do the magnitude and phase plots look like? 📊
- 3 What is the cutoff frequency? ⌚

Let's see those answers, engineers! 🧑🔧 ⚙️ 💡 #Engineering #InterviewPrep #ElectricalEngineering



Solution

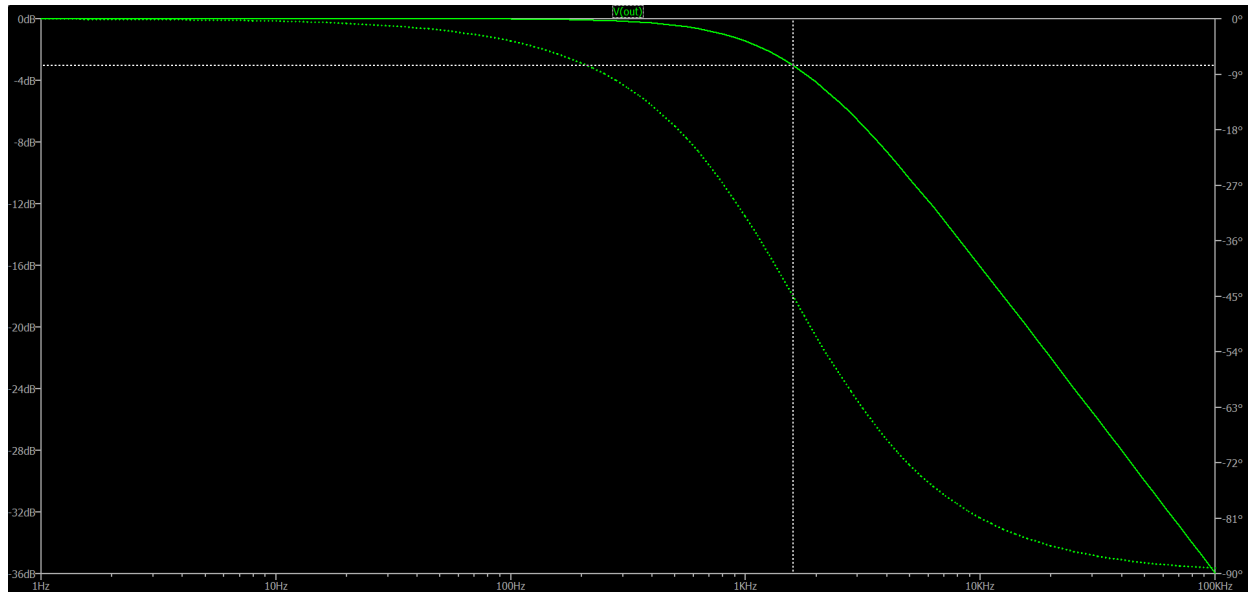- 1 What kind of filter is this? 🧑🔧
  - Low Pass Filter
- 2 What do the magnitude and phase plots look like? 📊



3 What is the cutoff frequency? 🕒

- 1.585kHz